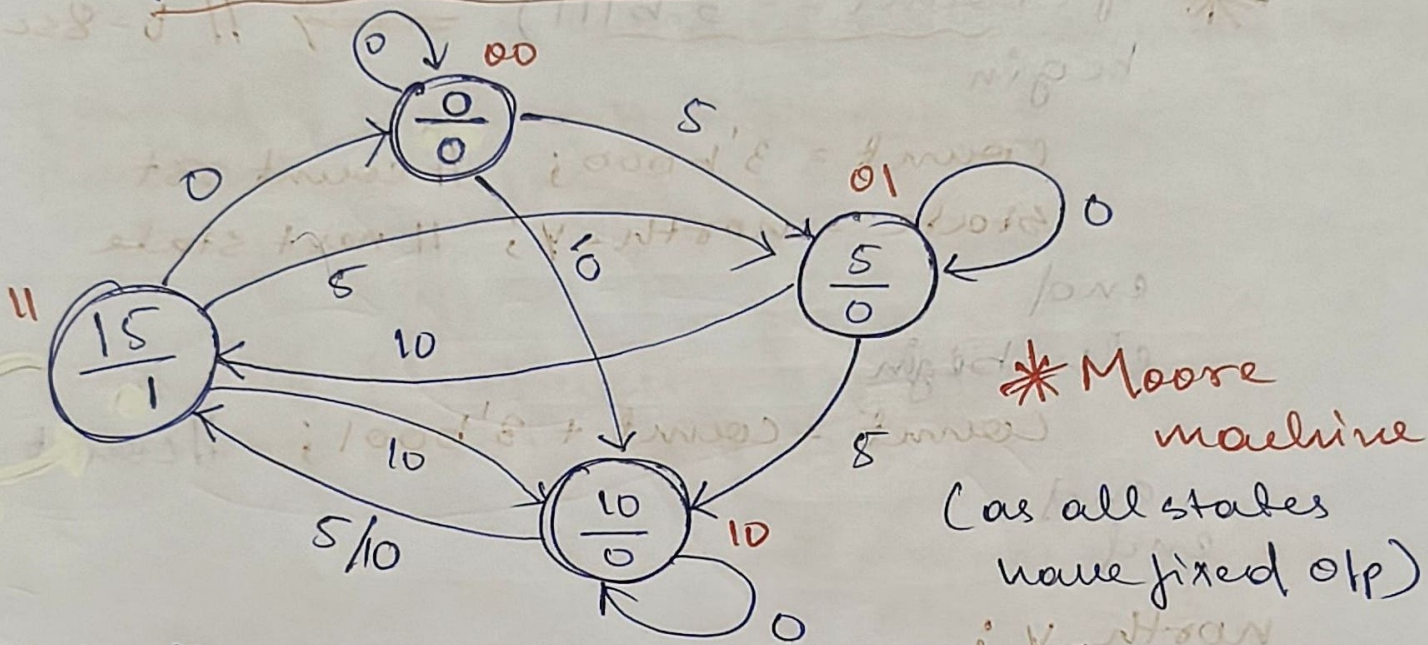


Vending Machine :- (based on eg)

- consider a vending machine only accepting the coins - 0, 5, 10 rs coins and when the accumulated value reaches 15 rs can is dispatched. (remember no money back!)
- The design accepts one coin per clock tick and update total accumulated accordingly



- Inputs :-
 - ① clk \rightarrow state update driving
 - ② rst \rightarrow sync rst
 - ③ coin[1:0] \rightarrow 2 bit coin code
(0 rs \rightarrow 00, 5 rs \rightarrow 01, 10 rs \rightarrow 10)
- O/p :- can-dispatch \rightarrow one when internal accumulated value = 15 rs
0 or else 0

Code Explanation :- (from the state dig.)

```
module vending-machine (  
    input clk, rst,  
    input [1:0] coin,  
    output can-despatch);
```

```
    reg [1:0] state, next_state;
```

```
    parameter S0 = 0; // 00
```

```
    parameter S1 = 1; // 01
```

```
    parameter S10 = 2; // 10
```

```
    parameter S15 = 3; // 11
```

// state :- holds current state

// next-state :- is a comb. helper that carries the next state

```
always @(posedge clk)
```

```
begin
```

```
    if (rst)
```

```
        state = S0;
```

// if clk is rst

```
    else
```

```
        state = next_state;
```

// otherwise → next state

```
end
```

```
always @(state, coin)
```

```
begin
```

```
    case (state)
```

```
        S0 : begin
```

```
            if (coin == 2'b00)
```

```
                next_state = S0;
```

```
            elsif (coin == 2'b01)
```

```
                next_state = S1;
```