

UART (Universal Asynch Tx & Rx) Communication Protocol

- A serial comms Protocol that allows device to exchange data without a shared clk signal
- It uses min. 2 wires (Tx and Rx) and requires both devices to agree on param. like Baud rate (speed) and data format beforehand

VART Tx (Transmitter) :-

⇒ Ports :- inp - clk, rst, start, data[7:0]
oup - tx (serial line, idle high)

⇒ Internal state :-

- Sending (1-bit): whether a Tx is in progress
- Count (4-bit): 0---9 indicates which bit is driven

is driven

0 → start bit (0) 1-8 → data bits $data[0] \dots data[7]$ (LSB 1st)
9 → stop bit (1)

→ Reset Behaviour : on reset tx = 1 (idle high)
sending = 0, count = 0

→ Start & Transmission

- on Rising clk

→ If start & ! sending - begin new transfer
(sending = 1, count = 0)

→ If sending :


- Drive tx according to count
- Increment count
- If count == 9 after increment, deassert sending (Tx finish)

→ Cycle Mapping :-

cycle 0 : start bit (tx = 0)

cycle 1 → 8 : data[0] → data[7]

 cycle 9 : stop bit (tx = 1) ⇒ sending clr



• UART Rx (Receiver)

→ ports :- inp - clk, rst, rx (serial inp)
- olp - data-out [7:0], done

→ Internal state :-

- receiving (1-bit) : true while frame is being sampled.
- count (4-bit) : 0...9 progress through frame
 - detect start - receiving = 1, count = 0
 - on subsequent clk
 - ▶ count == 1...8 ⇒ sample and store bits into data out [0..7]
 - ▶ count == 9 ⇒ interpret as stop bit, set done = 1, receiving = 0

⇒ Start detection :-

when not receiving ($rx = 0$) at clk edge, code treats it as start bit and begins sampling from next clock

⇒ Sampling discipline used

- The design samples rx once per bit at the rising clk edge
- The code assumes Tx & Rx share the same clk.

⇒ Cycle Mapping eg :-

clk edge N : detect $rx = 0 \rightarrow$ start (receiving = 1, count = 0)

clk edge N+1 : sample data bit 0 \rightarrow data_out[0] = rx

" " N+2 : " " " 1 \rightarrow data_out[1] = rx

" " " " " " " " " " " "

clk edge N+8 : sample data bit 7 \rightarrow data_out[7] = rx

clk edge N+9 : sample data STOP (done = 1, receiving = 0)

• waveform / timing analysis

Assume data = 0x A5 = 10100101 (MSB - LSB)

LSB first stream 10100101 \Rightarrow if $A6 = 10100110$ *

\rightarrow LSB 1st 01100101

Cycle Tx Rx Samples

0 start = 0 detect start ($Rx = 0$)

1 data[0] = 1 sample bit - 0 \rightarrow 1

2 data[1] = 0 sample bit - 1 \rightarrow 0

3 data[2] = 1 sample bit - 2 \rightarrow 1

4 data[3] = 0 sample bit - 3 \rightarrow 0

5 data[4] = 0 sample bit - 4 \rightarrow 0

6 data[5] = 1 sample bit - 5 \rightarrow 1

7 data[6] = 0 sample bit - 6 \rightarrow 0

data[7] = don

8 data[7] = 1 sample bit - 7 \rightarrow 1
9 STOP sample stop \rightarrow done = 1

• Practical Add-up

① Baud Rate generator :-

use baud-tick to advance count and sampling rather than clk

② Oversampling on Rx :-

when rx sampled eg 8x and 16x baud, detect start when rx = low, then sample data bits at mid bit.

③ Synchronize rx :-

use 2-stage synch flip-flop before rx to avoid Metastability.

④ Framing and parity :-

Add checks for stop bit = 1

optional add of parity gen/check

⑤ FIFO Buffer :-

Add small FIFO on Tx/Rx sides so CPU can push/pull bytes Async without missing data

⑥ Non-blocking updates in code

⑦ done handshake :-

instead of using one-cycle pulse, consider valid + ready handshake to avoid missed reads.